



FRENETIC
FEEL IT



FRENETIC

FULL BRIDGE TRANSFORMER DESIGN: KEY ASPECTS

The Full-Bridge topology is the most common topology in the industry for designs with a maximum power higher than 500W. In the last years, LLC (specially with new semiconductor technology, GaN and SiC) are becoming a trending topic but, the use of Full-Bridge is still very popular. In this app note it will briefly comment some key aspects to take in consideration for the design of the transformer. It will consider a secondary side with center tap, but it can be considered for a single secondary winding.

MODULATION AT FULL BRIDGE:

The Full-Bridge converter is typically modulated with PWM or Phase Shift modulations. This modulations apply to the transformer a waveform as presented in Figure 1. The input voltage is applied during the PW in positive and negative (in order to avoid saturation of the transformer) and a zero interval called dead time (DT) is common in these modulations.

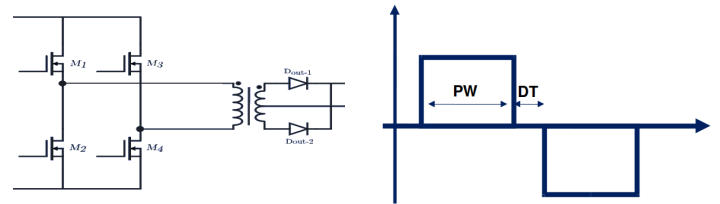


Figure 1. a) Full bridge topology with center tap. b) Transformer voltage waveform

TRANSFORMER KEY ASPECTS:

The key aspects to be presented in this app note are:

1. The importance of the leakage inductance.
2. The use of the magnetizing inductance for ZVS.

Leakage inductance (Llk) is very important for a lot of reasons, but only 3 will highlight here:

- ZVS: In order to achieve soft switching in the semiconductors (specially in MOSFET), we have to discharge the parasitic capacitance during the DT. The energy needed for discharging this capacitance is the energy stored in the Llk. That is $E_{LK} > E_{coss}$, where $E_{LK} = 0,5 \times L_{lk} \times I^2$. As it is observed, the energy depends on the current through the transformer and for this reason, at lower load states it is more difficult to achieve ZVS.

- Effective Duty Cycle Loss: As it is expected, including an inductance in series with an ideal transformer will affect the total energy transferred; this inductance limits the slope of the current and reduce the effective duty cycle applied to the transformer and therefore, the total energy transferred.

- Oscillations: The Llk resonates with the secondary side diode capacitance and its own transformer capacitance, this resonance can breakdown the diodes and provoke spikes if it is not limited. This problem can be solved modifying the resonant or including a snubber. The Figure 2 has been obtained using a non dissipative snubber for limiting the peaks.

The use of **magnetizing inductance (Lm)** for ZVS is a strategy that usually happens naturally, at low power levels, when the load main current energy stored in Llk is not enough for discharging the capacitances, the current through the LM helps. This current depends only on the voltage applied to the transformer. This strategy increase conduction losses and it is only recommended when the original transformer design has a very high value of LM and reducing it will not affect to the main behavior of the circuit.

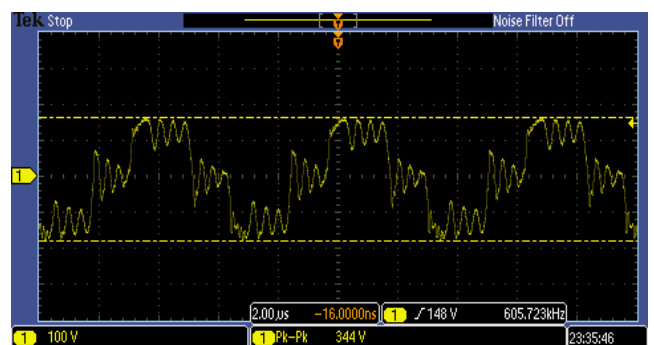


Figure 2. Transformer voltage with oscillations

CONCLUSIONS

Design a good full bridge transformer will help you to have a smooth project, with less EMI noise, reliability of the semiconductors and better efficiency. These key parameters are very important for a proper design.



Try Frenetic